
Estimating the BLA of MIMO sub-networks in simulations

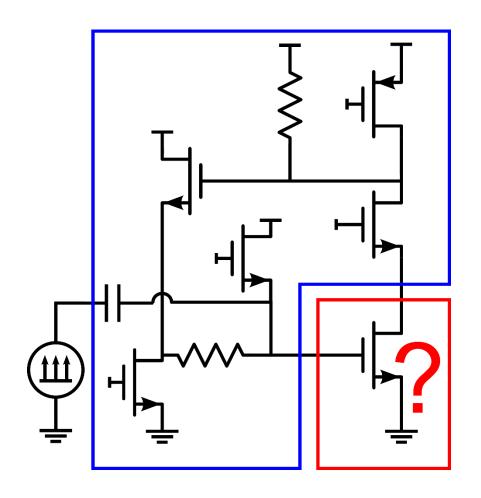
Adam Cooman, Ebrahim Louarroudi & Gerd Vandersteen






Electronic Circuits = MIMO network...



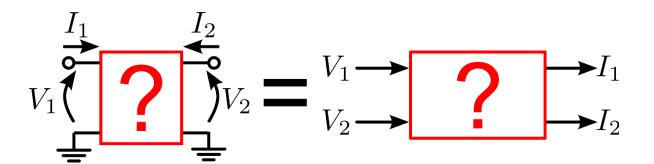


Excited by a single multisine

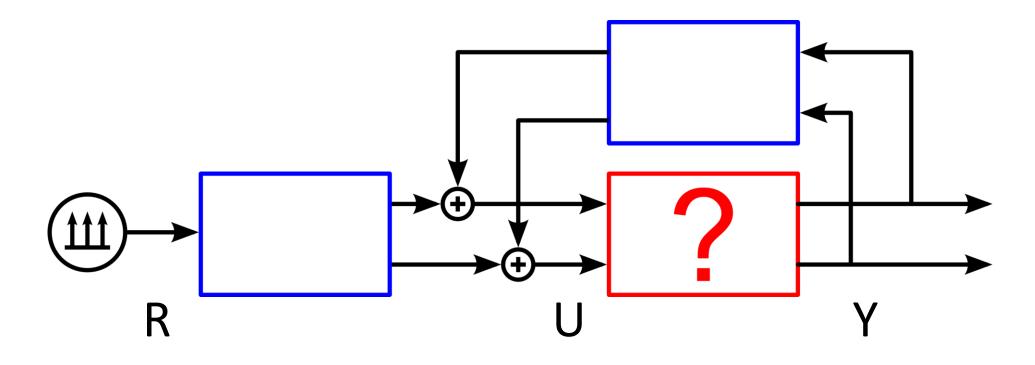

$$BLA_{?} = \frac{BLA_{R \to Y}}{BLA_{R \to U}}$$


Classic solution: Add extra multisine

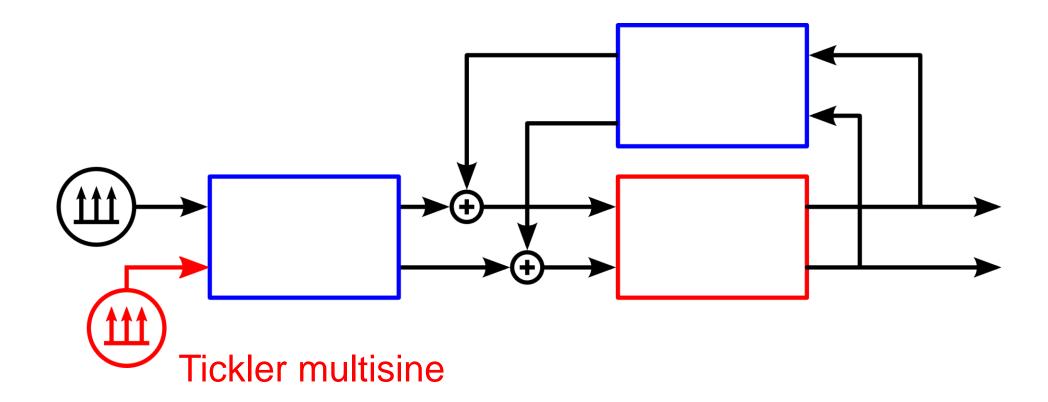


LSSS Analysis offers a solution

$$f(DC + \epsilon(t)) = f(DC) + \epsilon(t) \cdot \frac{d}{dx} f(x) \Big|_{x=DC}$$

$$f(LS(t) + \epsilon(t)) = f(LS(t)) + \epsilon(t) \cdot \frac{d}{dx} f(x) \Big|_{x=LS(t)}$$

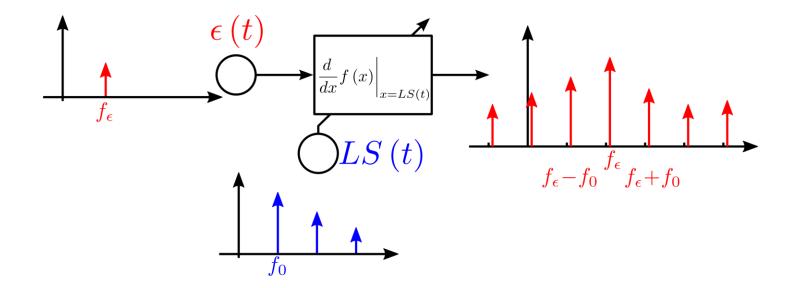


Small-signal sees the BLA as well

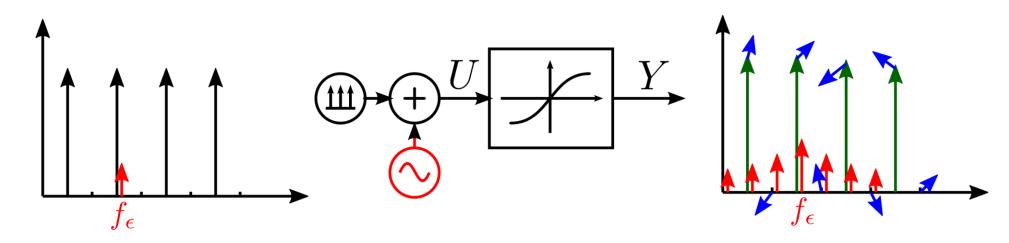


$$Y(f_k) = U(f_k) \cdot \left(G^{[1]}(f_k) + \sum_{i=-N}^{N} G^{[3]}(f_i, -f_i, f_k) \cdot |U(f_i)|^2 + \sum_{i=-N}^{N} \sum_{j=-N}^{N} G^{[3]}(f_i, f_j, f_k) \cdot U(f_i)U(f_j) \right)$$

$$Y(\mathbf{f_{\epsilon}}) = U(\mathbf{f_{\epsilon}}) \cdot \left(G^{[1]}(\mathbf{f_{\epsilon}}) + \sum_{i=-N}^{N} G^{[3]}(f_i, -f_i, \mathbf{f_{\epsilon}}) \cdot |U(f_i)|^2\right)$$


Example: CMOS amplifier

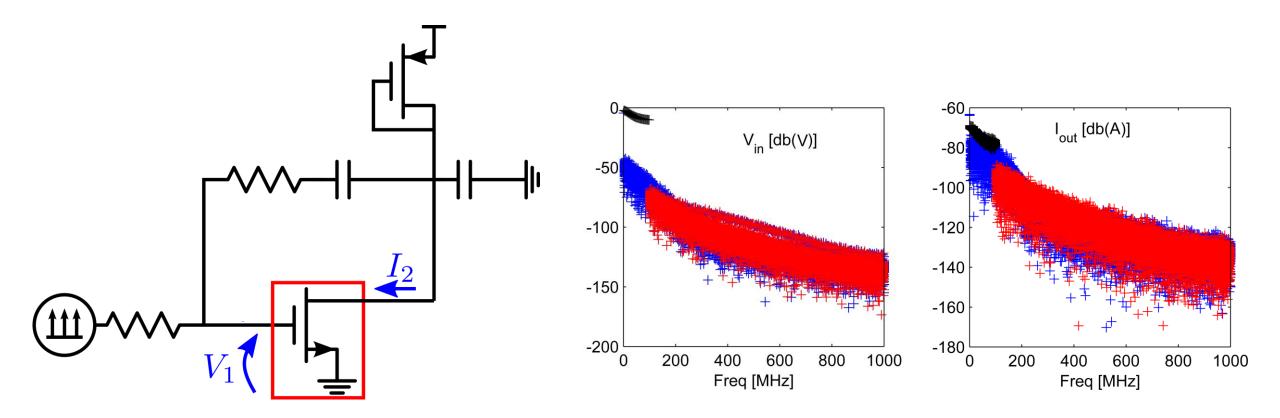


As expected, both techniques match

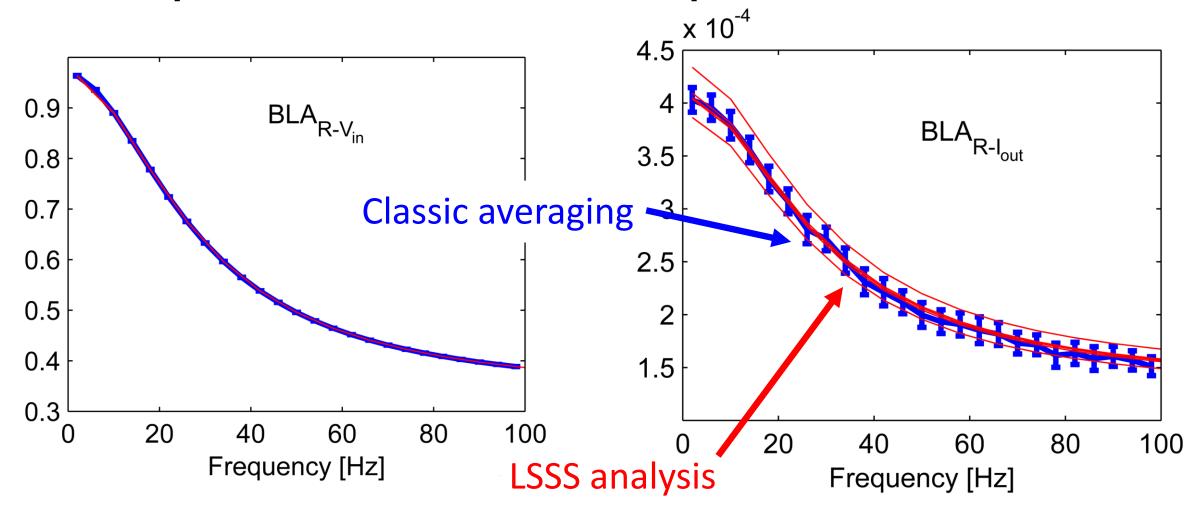


As expected, both techniques match

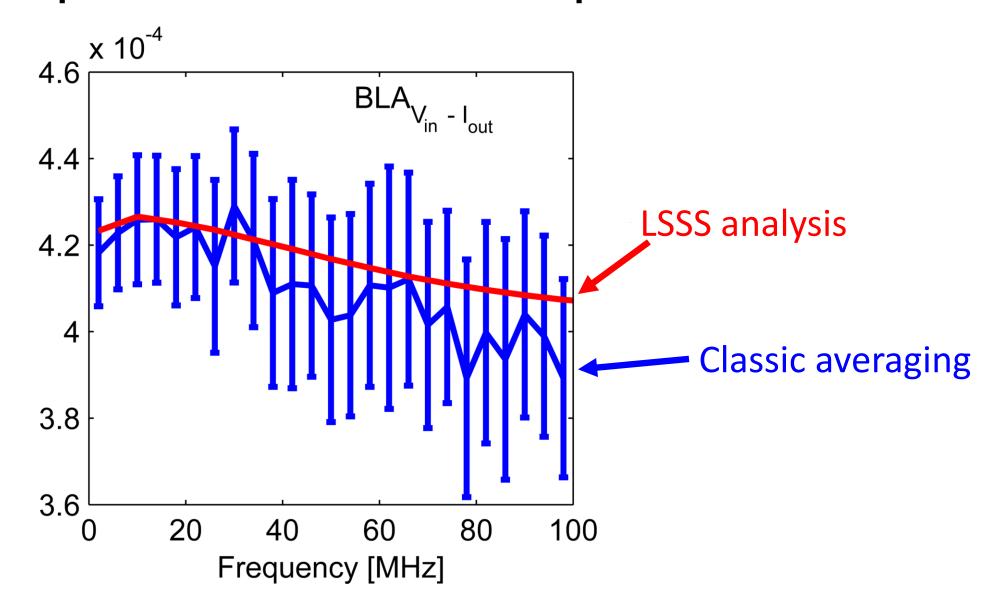


MIMO is just multiple experiments

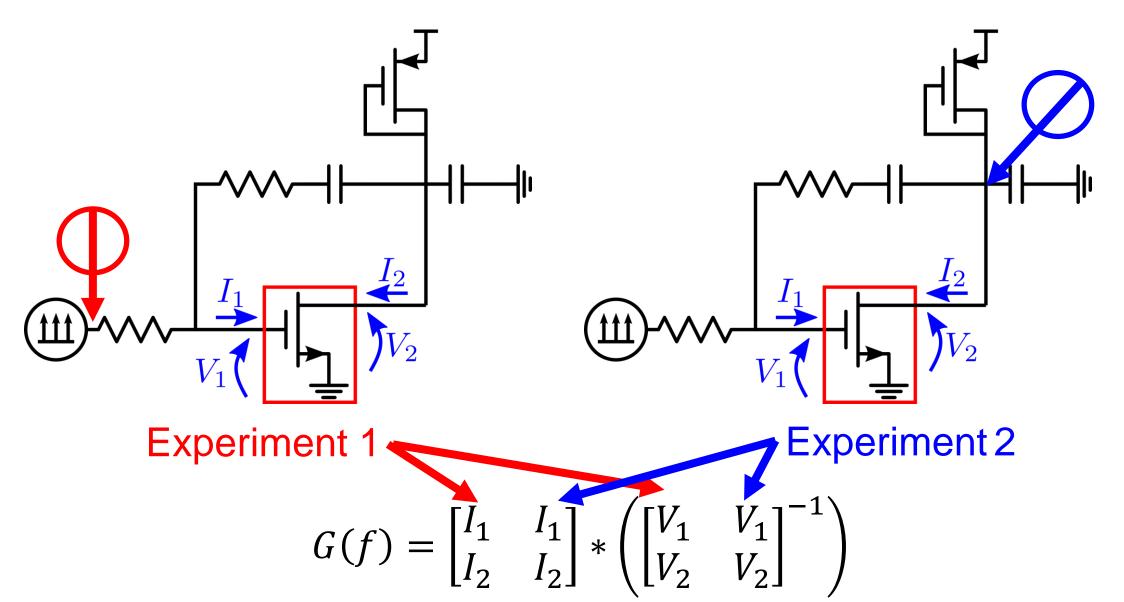

Back to the example

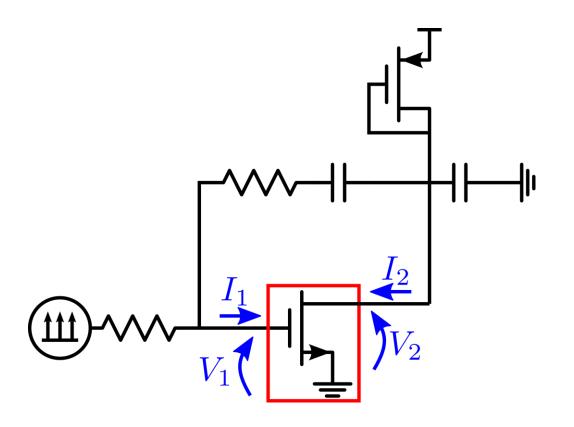

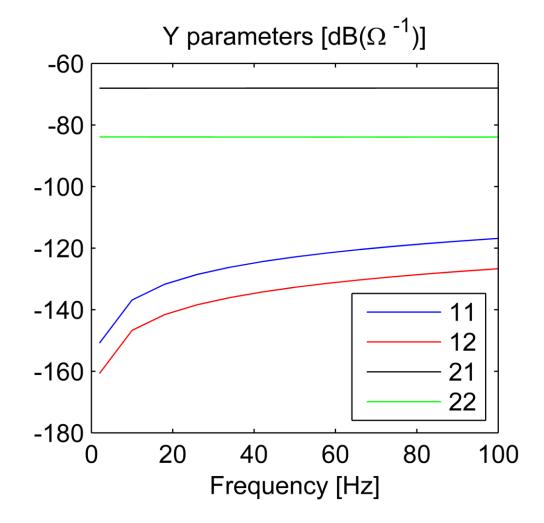

Conclusions

Linearisation around MS ⇒ tickler issues solved no danger of disturbing the operating point

Additional benefits

Single-tone excitation ⇒ flexible frequency grid Contributions are smooth ⇒ less MS phase realisations

But! you need access to Large-Signal Small-Signal simulation